

$$x_3 x_2 x_1 x_0 \% 4 = -0$$

# KARNAUGH

$$z = \bar{x}_1 + x_0$$

$$(x_0 + \overline{x}_1) \cdot (x_0 + \overline{x}_0)$$
 ~~$x + x_0$~~ 

$\{ \text{FA, MUX, DEMUX, CONFRONTATORE, CODIFICATORE, SHIFTER} \}^{\text{MUL}}$

|    |                |
|----|----------------|
| z  | $\forall \neq$ |
| 00 |                |
| 01 |                |
| 10 |                |
| 11 |                |
| k  |                |

| $x_3$ | $x_2$ | $x_1$ | $x_0$ | $z_1, z_0$ |
|-------|-------|-------|-------|------------|
| 1     | 0     | 0     | 0     | 0 0        |
| 0     | 1     | 0     | 0     | 0 1        |
| 0     | 0     | 1     | 0     | 1 0        |
| 0     | 0     | 0     | 1     | 1 1        |


$$Z_1 = \bar{X}_3 \bar{X}_2 X_1 \bar{X}_0 + \bar{X}_3 \bar{X}_2 \bar{X}_1 X_0$$

$$Z_2 = \bar{x}_3 x_2 \bar{x}_1 \bar{x}_0 + \bar{x}_3 \bar{x}_2 x_1 x_0$$


# SHIFTER

SHIFT  $\left\{ \begin{array}{l} \text{logici} \\ \text{aritmetici} \end{array} \right\} \rightarrow \begin{array}{l} ds \\ sn \end{array}$

## SHIFT LOGICI

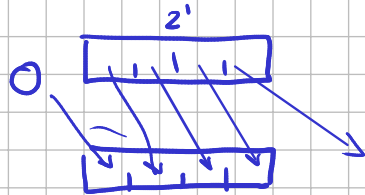

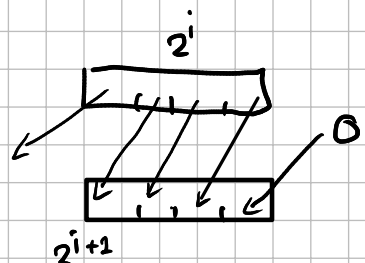
shift <sup>logici</sup> ds di 1 pos  $/2$



shift logico a sn di 1 pos  $*2$

## SHIFT ARITMETICI

~~sn~~ ds

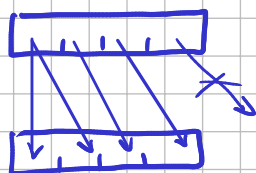

-3

$$2^{q-1} \dots 2^{h-1} - 1$$

$-3 \mid 0011$

1100

1101

1100

1110

0001

$-1$

0010

1100


0001

1


0010

-



## SHIFT LOG DS 1

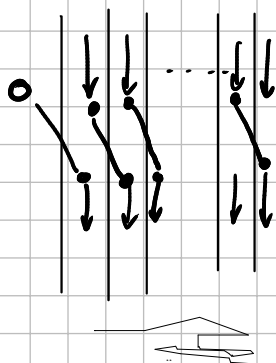

## OP SHIFT LOG a DS di K pos

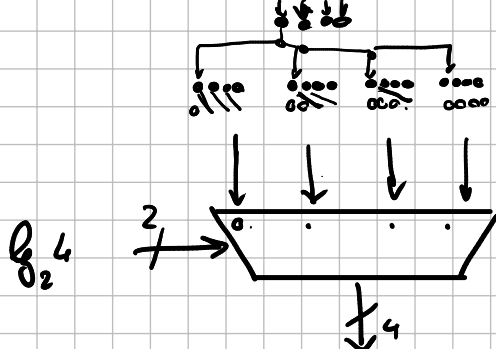

k=4

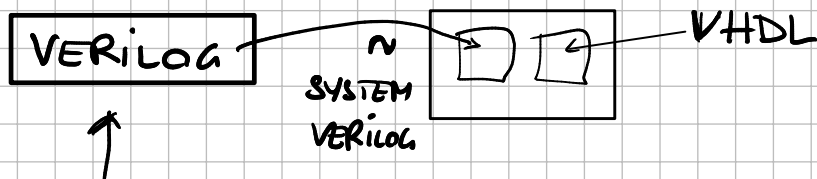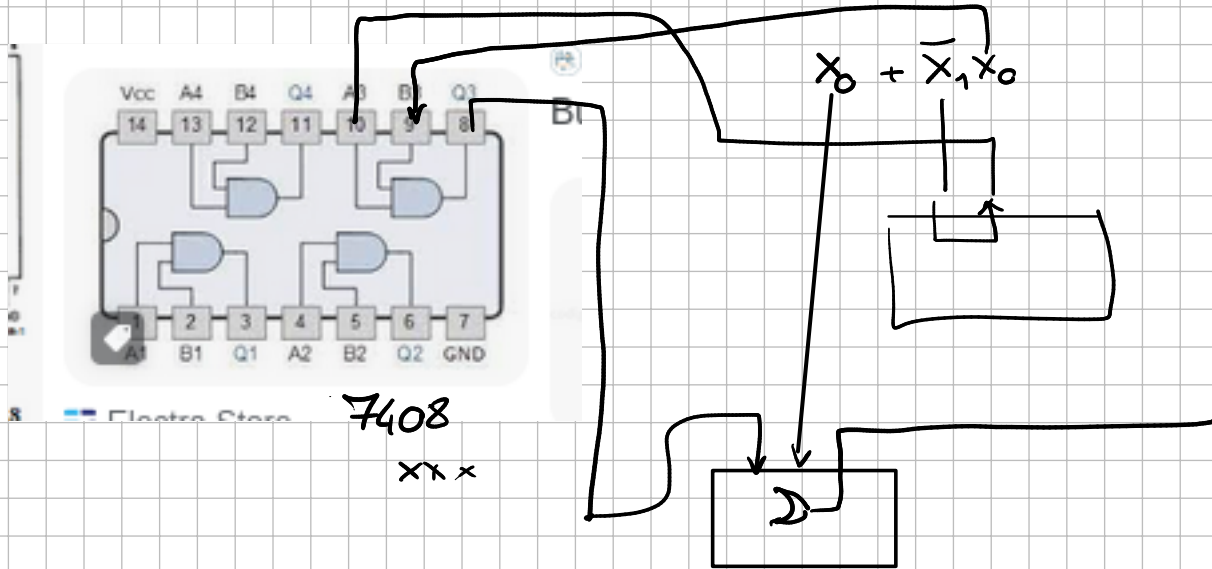

icarus verilog


## LOGICA COMBINATORIA FUNZIONI BOOLEANE

1 solo bit output  
PRIMITIVE name ( );


etichetta Verilog

ENDPRIMITIVE

MODULE name ( );

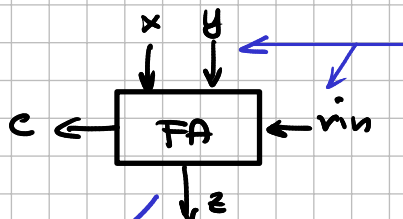

input x, input y,  
input rin,

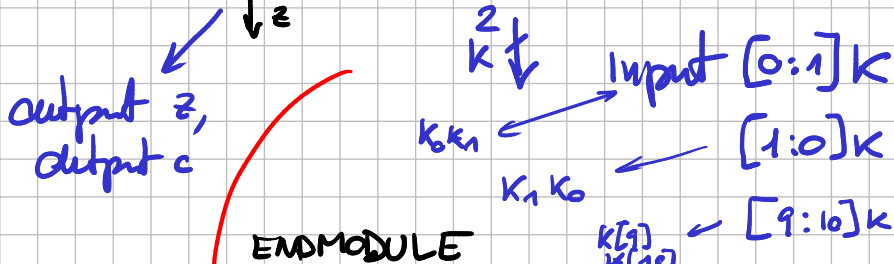

ENDMODULE

assign rout = expr bool  
dello usor  
di input

&&

AND

!

NOT

||

OR



assign z = (x && y) || (x && y);

TABLE

```

{ 0 0 0 : 0;
  0 0 1 : 1;
  1 1 1 : 1;
}
ENDTABLE

```

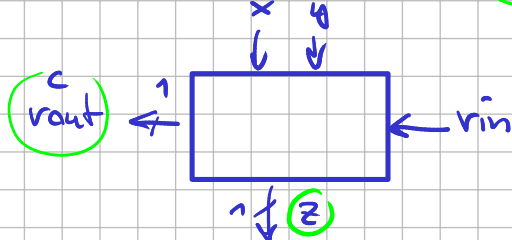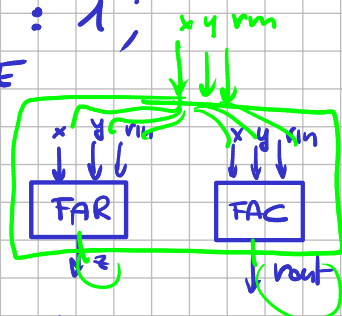


TV CO

| $x_3 x_2 x_1 x_0$ | $z_1 z_0$ |
|-------------------|-----------|
| 1 0 0 0           | 0 0       |
| 0 1 0 0           | 0 1       |
| 0 0 1 0           | 1 0       |
| 0 0 0 1           | 1 1       |

4 ingressi da 1 bit

$2^4$  righe

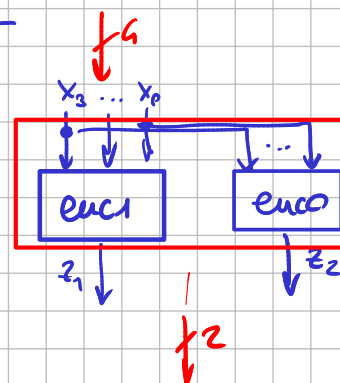

$$z_1 = \bar{x}_3 \bar{x}_2 x_1 \bar{x}_0 + \bar{x}_3 \bar{x}_2 \bar{x}_1 x_0$$

$$z_2 = \bar{x}_3 x_2 \bar{x}_1 \bar{x}_0 + \bar{x}_3 x_2 x_1 x_0$$

$x_1 x_0 \geq y_1 y_0$

f: qual'è il più grande di 2 numeri a 2 bit

| $x_1 x_0$ | $y_1 y_0$ | $z_1 z_0$ |
|-----------|-----------|-----------|
| 0 0       | 0 0       | 0 0       |
|           | 0 1       | 0 1       |
|           | 1 0       | 1 0       |
|           | 1 1       | 1 1       |
| 0 1       | 0 0       | 0 1       |
|           | 0 1       | 0 1       |
|           | 1 0       | 1 0       |
|           | 1 1       | 1 1       |
| 1 0       |           |           |
| 1 1       |           |           |

| $x_1 x_0$ | $y_1 y_0$ | $z_1$ |
|-----------|-----------|-------|
| 0 0       | 0 0       | 0     |
| 0 0       | 0 1       | 0     |
| 0 0       | 1 0       | 1     |
| 0 0       | 1 1       | 1     |
| 0 1       | 0 0       | 0     |
| 0 1       | 0 1       | 0     |
| 0 1       | 1 0       | 1     |
| 0 1       | 1 1       | 1     |
| 1 0       | 0 0       | 1     |
| 1 0       | 0 1       | 1     |
| 1 0       | 1 0       | 1     |
| 1 0       | 1 1       | 1     |

| $x_1 x_0$ | $y_1 y_0$ | $z_0$ |
|-----------|-----------|-------|
| 0 0       | 0 0       | 0     |
| 0 0       | 0 1       | 1     |
| 0 0       | 1 0       | 1     |
| 0 0       | 1 1       | 0     |
| 0 1       | 0 0       | 1     |
| 0 1       | 0 1       | 1     |
| 0 1       | 1 0       | 1     |
| 0 1       | 1 1       | 0     |
| 1 0       | 0 0       | 1     |
| 1 0       | 0 1       | 1     |
| 1 0       | 1 0       | 1     |
| 1 0       | 1 1       | 1     |

$$z_1 = x_1 + y_1$$

$$z_2 = x_1 x_0 + y_1 y_0 + \bar{x}_0 y_0 + x_0 \bar{y}_1$$

module maggiore di (output [1:0] z,  
input [1:0] x, input [1:0] y);