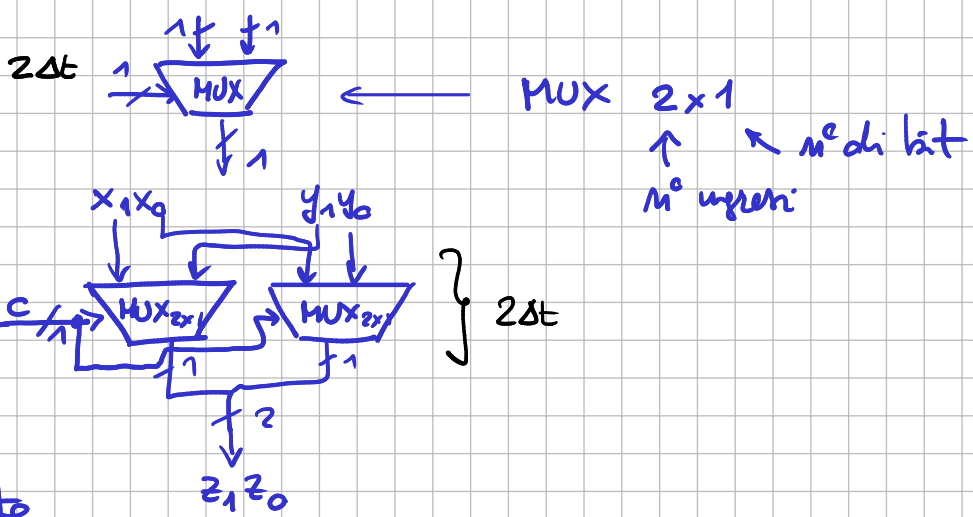


ESERCIZI

MUX



per passare
sull'uscita
l'ingresso di 2
bit scelto
dell'ingresso di
controllo

1)

TAB VERITÀ

c	x ₁	x ₀	y ₁	y ₀	z ₁ z ₀
0	x ₁	x ₀	-	-	x ₁ x ₀
1	-	-	y ₁	y ₀	y ₁ y ₀


c	x ₁	x ₀	y ₁	y ₀	z ₁ z ₀
0	0	0	-	-	0 0
0	0	1	-	-	0 1
0	1	0	-	-	1 0
0	1	1	-	-	1 1
1	-	-	0	0	0 0
1	-	-	0	1	0 1
1	-	-	1	0	1 0
1	-	-	1	1	1 1

$$z_2 = \bar{c} \bar{x}_1 x_0 + \bar{c} x_1 x_0 + c y_0$$

$$z_0 = \bar{c} x_0 + c y_0$$

$$z_1 = \bar{c} x_1 \bar{x}_0 + \bar{c} x_1 x_0 + c y_1 \bar{y}_0 + c y_1 y_0 =$$

$$z_1 = \bar{c} x_1 + c y_1$$

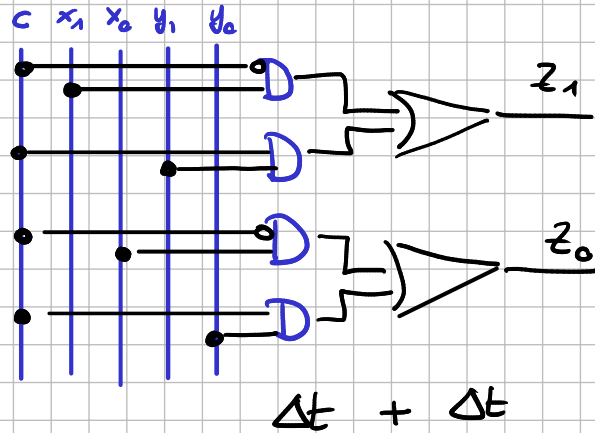

C	x ₁	x ₀	y ₁	y ₀	z ₁	z ₀
0	0	0	-	-	0	0
0	0	1	-	-	0	1
0	1	0	-	-	1	0
0	1	1	-	-	1	1
1	-	-	0	0	0	0
1	-	-	0	1	0	1
1	-	-	1	0	1	0
1	-	-	1	1	1	1

C=0

x ₁ x ₀	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1



$\bar{C}x_1 \uparrow$

C=1

x ₁ x ₀	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$Cy_1 \leftarrow$

(z₁)

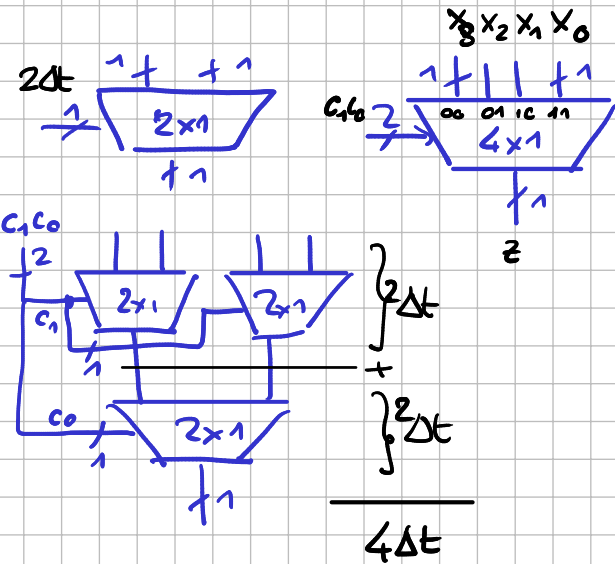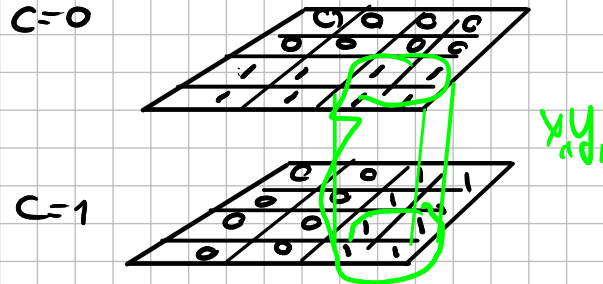

C ₁	C ₀	x ₃	x ₂	x ₁	x ₀	z
0	0	1	-	-	-	1
0	0	0	-	-	-	0
0	1	-	1	-	-	1
1	0	-	-	1	-	1
1	1	-	-	-	1	1

$$z = \bar{C}_1 \bar{C}_0 x_3 + \bar{C}_1 C_0 x_2 + C_1 \bar{C}_0 x_1 + C_1 C_0 x_0$$

6 ingressi
termini AND
di 3 ingressi

← 0 ⇒ no termine AND

$$2 = \lceil \log_2 4 \rceil \leftarrow \text{OR di 4 ingressi ciascuno}$$

$$2 = \lceil \log_2 3 \rceil \leftarrow \text{AND di 3 ingressi}$$

4 Δt

quanti livelli di logica?
(con parte di 2 ingressi)

MUX 2x1


C	x	y	z
0	1	-	1
1	-	1	1

$$z = \bar{C}x + Cy$$

OR di 2 ingressi
ciascuno AND di 2 ingressi

2 Δt con ←

DEMUX

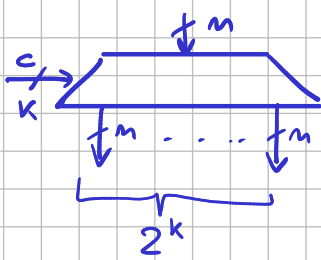

$C \ X$	$z_1 z_0$
0 1	1 0
1 1	0 1

$$z_1 = \bar{C} X$$

$$z_2 = C X$$



1 liv logico

1 Δt

} ↓

} ↓

2 Δt

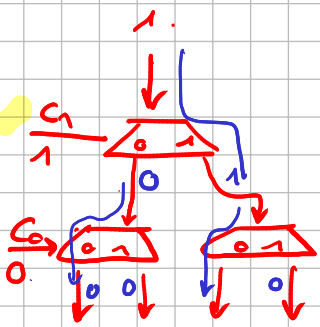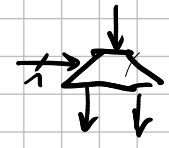

DEMUX 1bit su 4 uscite

$C_1 C_0 \ X$	$z_3 z_2 z_1 z_0$
0 0 1	1 0 0 0
0 1 1	0 1 0 0
1 0 1	0 0 1 0
1 1 1	0 0 0 1

$$z_3 = \bar{C}_1 \bar{C}_0 X$$

$$z_2 = \bar{C}_1 C_0 X$$


$$z_1 = C_1 \bar{C}_0 X$$

$$z_0 = C_1 C_0 X$$

porta da 2 ingressi

2 livelli di logico (AND)



$$\bar{C}_1 \bar{C}_0 X$$

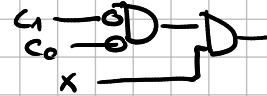

2 Δt

VS

CONFRONT AT ORE

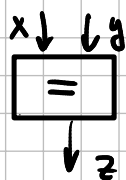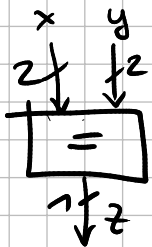

$$x=y \Rightarrow z=1$$

$$\text{else } z=0$$

$x_1 x_0 y_1 y_0$	z
00 00	1
01 01	1
10 10	1
11 11	1

$x y$	z
00	1
01	0
10	0
11	1

$$z = \bar{x}\bar{y} + xy$$


2 livelli di logica
(2 Δt)

$$z = (\bar{x}_1 \bar{x}_0) \bar{y}_1 \bar{y}_0 + (\bar{x}_1 x_0) \bar{y}_1 y_0 +$$

$$x_1 \bar{x}_0 y_1 \bar{y}_0 + x_1 x_0 y_1 y_0$$


4 livelli di logica

2 bit

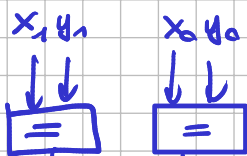

liv di logica ? x n bit

n bit

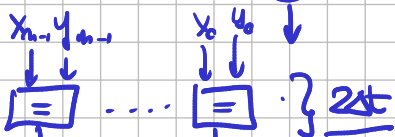

TV

$$\left\{ \begin{matrix} m+n & z \end{matrix} \right\} 2^m \text{ "1"}$$

$$\left\lceil \lg_2(2m) \right\rceil + \left\lceil \lg_2(2^n) \right\rceil$$

AND OR

$$\left\lceil \lg_2(2m) \right\rceil + m$$


$n=4$

$x_3 x_2 x_1 x_0$	$y_3 y_2 y_1 y_0$	z
0000	0000	1
0001	0000	0
0010	0000	0
0011	0000	0

$$\left\{ \begin{matrix} 24 \\ 16 \end{matrix} \right\}$$


$$\left\{ \begin{matrix} 1 \\ 1 \\ 1 \\ 1 \end{matrix} \right\} 2^m$$

2Δt bat

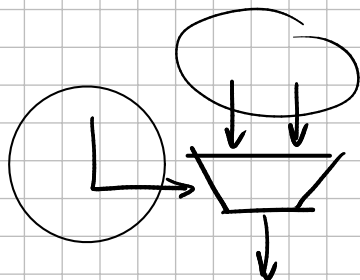

$$\max \{a\Delta t, b\Delta t\}$$


$$+ t_{mux}$$

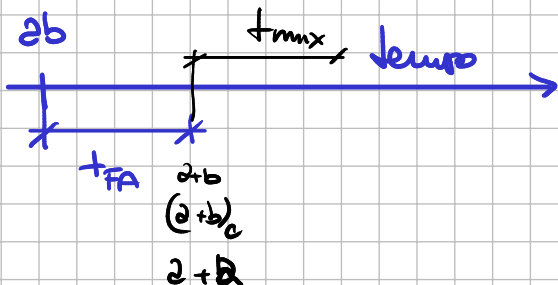


if (a+b is pari) → a+b
else a+a

tFA

tmax

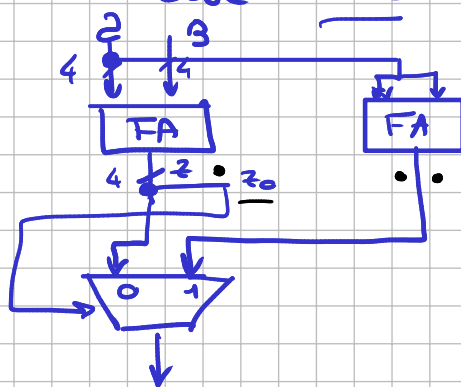

if (i bit di a+b = a+a) ==

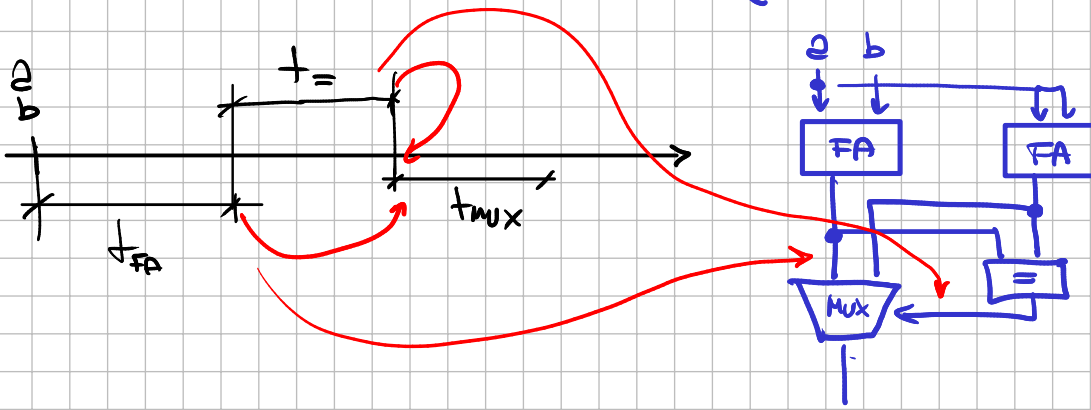

$f(x) = \underline{\text{se}(x \text{ pari})} \} \text{ se } x \text{ (divisibile } \times 4) \text{ then } \underline{z = 1}$
 $\times 4 \text{ bit} \quad \text{else } \underline{z = 0}$

8	4	2	1	
x_3	x_2	x_1	x_0	z
-	-	-	1	1
0	0	0	0	1
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1

4 bit $\Rightarrow [0, 15]$

0
4
8
12

2 livelli di logica

$$z = x_0 + \bar{x}_3 \bar{x}_1 \bar{x}_0 + x_3 \bar{x}_1 \bar{x}_0 = \underline{x_0 + \bar{x}_1 \bar{x}_0}$$

upper bound livelli di logica? (con porta da 2 ingressi)

$2^n \} \frac{2^n}{2}$

$z = \text{OR di } \frac{2^n}{2} (2^{n-1}-1) \text{ ingressi ciascuno}$
 $\text{AND di } n \text{ bit}$

$$\left\lceil \lg_2(2^{n-1}) \right\rceil + \left\lceil \lg_2 n \right\rceil$$

n

OR

AND

$n=4$

$$4 + 2 = 6$$

x_3	x_2	x_1	x_0	z
-	-	-	1	1
0	0	0	0	1
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1



$x_3 x_2$	00	01	11	10
00	1	1	1	0
01	1	1	1	0
11	1	1	1	0
10	1	1	1	0

$$z = \bar{x}_1 + x_0$$

$f(x) = \text{se}(x_{\text{pari}}) \times 4 \text{ bit}$

$\text{se}(x_{\text{pari}}) = \begin{cases} \text{se} \times (\text{divisible} \times 4) & \text{then } z = 1 \\ \text{else } z = 0 \end{cases}$

$\text{else } z = 1$

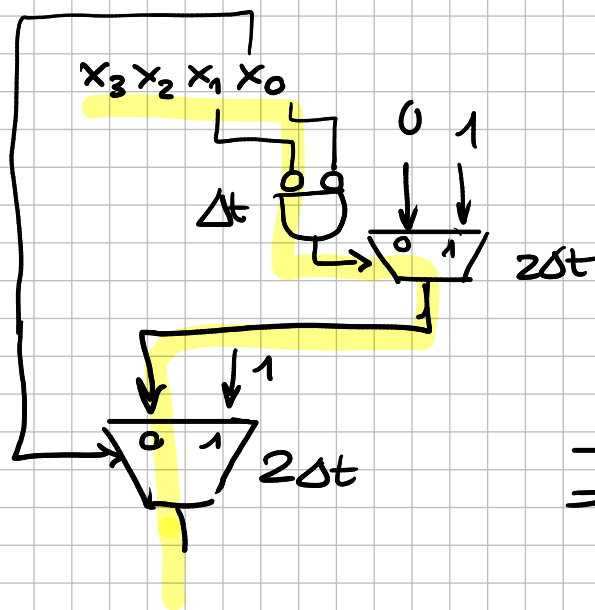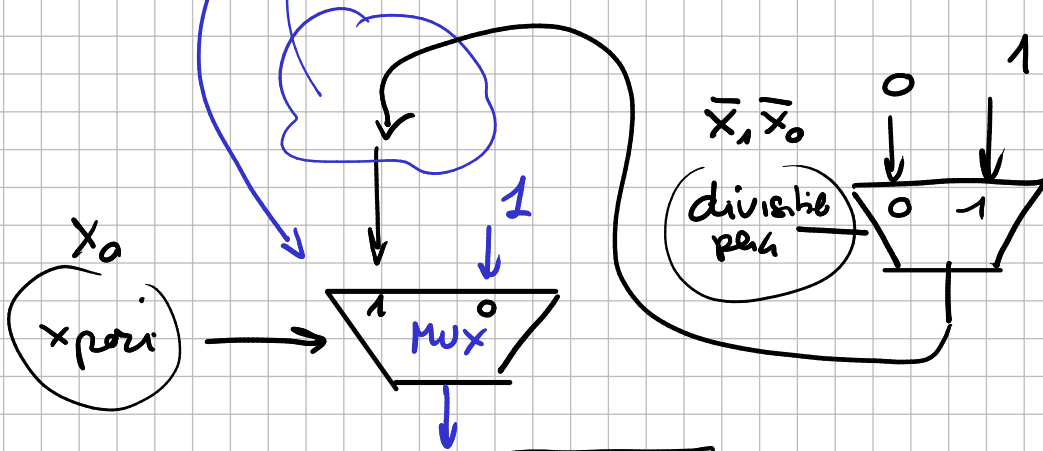

$f_{\text{mux}} = 2\Delta t$

$$\begin{aligned}
 & \Delta t + 2\Delta t + 2\Delta t \\
 & \hline
 & = 5\Delta t
 \end{aligned}$$